

Name:

For the circuit shown below find the transfer function $\frac{V_R(s)}{V(s)}$ in terms of R , L , and C .

